



Chapter 7

Memory and Programmable Logic

7-1




Outline

- Introduction
- Random-Access Memory
- Memory Decoding
- Error Detection and Correction
- Read-Only Memory
- Programmable Devices
- Sequential Programmable Devices

7-2

Mass Memory Elements

 - Memory is a collection of binary cells together with associated circuits needed to transfer information to or from any desired location



- Two primary categories of memory:
 - Random access memory (RAM)
 - Read only memory (ROM)

7-3

Programmable Logic Device

- The binary information within the device can be specified in some fashion and then embedded within the hardware
 - Most of them are programmed by breaking the fuses of unnecessary connections
- Four kinds of PLD are introduced
 - Read-only memory (ROM)
 - Programmable logic array (PLA)
 - Programmable array logic (PAL)
 - Field-programmable gate array (FPGA)

7-4

Outline

- Introduction
- Random-Access Memory
- Memory Decoding
- Error Detection and Correction
- Read-Only Memory
- Combinational Programmable Devices
- Sequential Programmable Devices

7-5

Random Access Memory

- A **word** is the basic unit that moves in and out of memory
 - The length of a word is often multiples of a byte (=8 bits)
- Memory units are specified by its **number of words** and the **number of bits** in each word
 - Ex: 1024(words) x 16(bits)
 - Each word is assigned a particular **address**, starting from 0 up to $2^k - 1$ (k = number of address lines)

Memory address		Memory content
Binary	decimal	
000000000	0	1011010101011101
000000001	1	1010101110001001
000000010	2	0000110101000110
	⋮	⋮
111111101	1021	100110100010100
111111110	1022	0000110100011110
111111111	1023	110111000100101

Fig. 7-3 Content of a 1024 × 16 Memory

7-6



Write and Read Operations

- Write to RAM
 - Apply the binary address of the desired word to the **address lines**
 - Apply the data bits that must be stored in memory to the **data input lines**
 - Activate the **write control**
- Read from RAM
 - Apply the binary address of the desired word to the **address lines**
 - Activate the **read control**

7-7

Timing Waveforms

  - CPU clock = 50 MHz
 - cycle time = 20 ns
- Memory access time = 50 ns
 - The time required to complete a read or write operation
- The control signals must stay active for at least 50 ns
 - 3 CPU cycles are required



7-8

Types of Memories

- Access mode:
 - Random access: any locations can be accessed in any order
 - Sequential access: accessed only when the requested word has been reached (ex: hard disk)
- Operating mode:
 - Static RAM (SRAM)
 - Dynamic RAM (DRAM)
- Volatile mode:
 - Volatile memory: lose stored information when power is turned off (ex: RAM)
 - Non-volatile memory: retain its storage after removal of power (ex: flash, ROM, hard-disk, ...)

7-9

SRAM vs. DRAM

- | | |
|---|---|
| <ul style="list-style-type: none"> ■ Static RAM: <ul style="list-style-type: none"> ■ Use internal latch to store the binary information ■ Stored information remains valid as long as power is on ■ Shorter read and write cycles ■ Larger cell area and power consumption | <ul style="list-style-type: none"> ■ Dynamic RAM: <ul style="list-style-type: none"> ■ Use a capacitor to store the binary information ■ Need periodically refreshing to hold the stored info. ■ Longer read and write cycles ■ Smaller cell area and power consumption |
|---|---|

 


Fig. 6-5 Static RAM Cell

 



Fig. 6-12 Dynamic RAM Cell, Hydraulic Analogy of Cell Operation, and Cell Model

Outline

- Introduction
- Random-Access Memory
- **Memory Decoding**
- Error Detection and Correction
- Read-Only Memory
- Combinational Programmable Devices
- Sequential Programmable Devices

7-11

Memory Construction

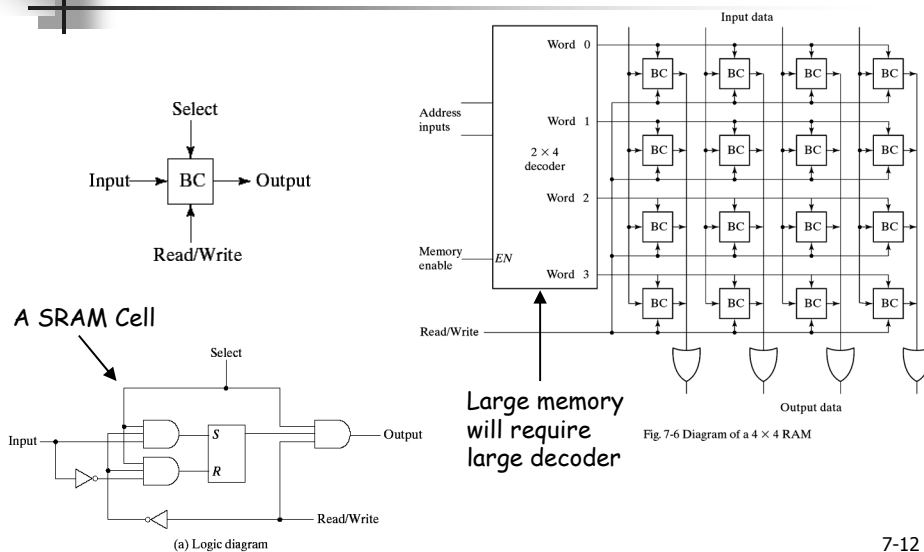

7-12

Coincident Decoding

- Address decoders are often divided into two parts
 - A two-dimensional scheme
- The total number of gates in decoders can be reduced
- Can arrange the memory cells to a square shape
- EX: 10-bit address
 $404 = 0110010100$
 $X = 01100$ (first five)
 $Y = 10100$ (last five)

 


Fig. 7-7 Two-Dimensional Decoding Structure for a 1K-Word Memory

7-13

Address Multiplexing

- Memory address lines often occupy too much I/O pads
 - $64K = 16$ lines
 - $256M = 28$ lines
- Share the address lines of X and Y domains
 - Reduce the number of lines to a half
 - An extra register is required for both domain to store the address
- Two steps to send address
 - $RAS=0$: send row address
 - $CAS=0$: send column address

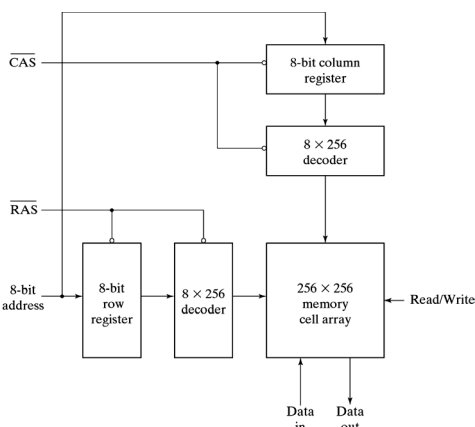


Fig. 7-8 Address Multiplexing for a 64K DRAM

7-14

Outline

- Introduction
- Random-Access Memory
- Memory Decoding
- Error Detection and Correction
- Read-Only Memory
- Combinational Programmable Devices
- Sequential Programmable Devices

7-15

Error Detection & Correction

- Memory arrays are often very huge
 - May cause occasional errors in data access
- Reliability of memory can be improved by employing error-detecting and correcting codes
- Error-detecting code: only check for the **existence** of errors
 - Most common scheme is the parity bit
- Error-correcting code: check the existence and **locations** of errors
 - Use multiple parity check bits to generate a **syndrome** that can indicate the erroneous bits
 - Complement the erroneous bits can correct the errors

7-16

Hamming Code (1/2)

- k parity bits are added to an n-bit data word
- The positions numbered as a **power of 2** are reserved for the parity bits
 - Ex: original data is 11000100 (8-bit)
 - ⇒ Bit position: **1 2 3 4 5 6 7 8 9 10 11 12**
 $P_1 \ P_2 \ 1 \ P_4 \ 1 \ 0 \ 0 \ P_8 \ 0 \ 1 \ 0 \ 0$
 - $P_1 = \text{XOR of bits } (3,5,7,9,11) = 0$
 - $P_2 = \text{XOR of bits } (3,6,7,10,11) = 0$
 - $P_4 = \text{XOR of bits } (5,6,7,12) = 1$
 - $P_8 = \text{XOR of bits } (9,10,11,12) = 1$
 - The composite word is 001110010100 (12-bit)

7-17

Hamming Code (2/2)

- When the 12 bits are read from memory, the parity is checked over the **same combination** of bits **including** the parity bit
 - $C_1 = \text{XOR of bits } (1,3,5,7,9,11)$
 - $C_2 = \text{XOR of bits } (2,3,6,7,10,11)$
 - $C_4 = \text{XOR of bits } (4,5,6,7,12)$
 - $C_8 = \text{XOR of bits } (8,9,10,11,12)$
 - $(001110010100) \rightarrow C = C_8 C_4 C_2 C_1 = 0000$: no error
 - $(101110010100) \rightarrow C = C_8 C_4 C_2 C_1 = 0001$: bit 1 error
 - $(001100010100) \rightarrow C = C_8 C_4 C_2 C_1 = 0101$: bit 5 error

viewed as a binary number $\xrightarrow{\quad}$

7-18

General Rules of Hamming Code

- The number of parity bits:
 - The syndrome C with k bits can represent $2^k - 1$ error locations (0 indicates no error)
 - $2^k - 1 \geq n + k \rightarrow 2^k - 1 - k \geq n$

Number of Check Bits, k	Range of Data Bits, n
3	2-4
4	5-11
5	12-26
6	27-57
7	58-120

- The members of each parity bit:
 - C1(P1): have a "1" in **bit 1** of their location numbers
1(000**1**), 3(00**11**), 5(010**1**), 7(01**11**), 9(100**1**), ...
 - C2(P2): have a "1" in **bit 2** of their location numbers
2(00**10**), 3(00**11**), 6(01**10**), 7(01**11**), 10(10**10**), ...
 - C: with parity bit; P: without parity bit itself

7-19

Extension of Hamming Code

- Original Hamming code can detect and correct only a **single error**
 - Multiple errors are not detected
- Add an extra bit as the parity of total coded word
 - Ex: 001110010100P₁₃ (P₁₃=XOR of bits 1 to 12)
 - Still single-error correction but double-error detection
- Four cases can occur:
 - If C=0 and P=0, no error occurred
 - If C≠0 and P=1, single error occurred (can be fixed)
 - If C≠0 and P=0, double error occurred (cannot be fixed)
 - If C=0 and P=1, an error occurred in the P₁₃ bit

7-20

Outline

- Introduction
- Random-Access Memory
- Memory Decoding
- Error Detection and Correction
- **Read-Only Memory**
- Combinational Programmable Devices
- Sequential Programmable Devices

7-21

Read Only Memory

- A memory device that can permanently keep binary data
 - Even when power is turned off and on again

- For a $2^k \times n$ ROM,

it consists of

- k inputs (address line) and n outputs (data)
- 2^k words of n-bit each
- A $k \times 2^k$ decoder (generate all minterms)
- n OR gates with 2^k inputs
- Initially, all inputs of OR gates and all outputs of the decoder are fully connected

 


Fig. 7-10 Internal Logic of a 32×8 ROM

7-22

Programming the ROM

- Each intersection (crosspoint) in the ROM is often implemented with a fuse
- Blow out unnecessary connections according to the truth table
 - "1" means connected (marked as X)
 - "0" means unconnected
- Cannot recovered after programmed

 



Fig. 7-11 Programming the ROM According to Table 7-3

7-23

Design Comb. Circuit with ROM

- Derive the truth table of the circuit
- Determine minimum size of ROM
- Program the ROM

Inputs			Outputs					Decimal	
A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂	B ₁		B ₀
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

 

(a) Block diagram

A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

7-24

Types of ROMs

- Mask programming
 - Program the ROM in the semiconductor factory
 - Economic for large quantity of the same ROM
- Programmable ROM (PROM)
 - Contain all fuses at the factory
 - Program the ROM by burning out the undesired fuses (irreversible process)
- Erasable PROM (EPROM)
 - Can be restructured to the initial state under a special ultra-violet light for a given period of time
- Electrically erasable PROM (EEPROM or E²PROM)
 - Like the EPROM except being erased with electrical signals

7-25

Programmable Logic Devices

- ROM provides full decoding of variables
 - Waste hardware if the functions are given
- For known combinational functions, Programmable Logic Devices (PLD) are often used
 - Programmable read-only memory (PROM)
 - Programmable array logic (PAL)
 - Programmable logic array (PLA)
- For sequential functions, we can use
 - Sequential (simple) programmable logic device (SPLD)
 - Complex programmable logic device (CPLD)
 - Field programmable gate array (FPGA) ← most popular


7-26

Outline


- Introduction
- Random-Access Memory
- Memory Decoding
- Error Detection and Correction
- Read-Only Memory
- **Combinational Programmable Devices**
- Sequential Programmable Devices

7-27


Configurations of Three PLDs

 

(a) Programmable read-only memory (PROM)

 

(b) Programmable array logic (PAL)

 

(c) Programmable logic array (PLA)

Fig. 7-13 Basic Configuration of Three PLDs


7-28

Programmable Logic Array

- PLA does not provide full decoding of the variables
 - Only generate the terms you need
- The decoder is replaced by an array of AND gates that can be programmed

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

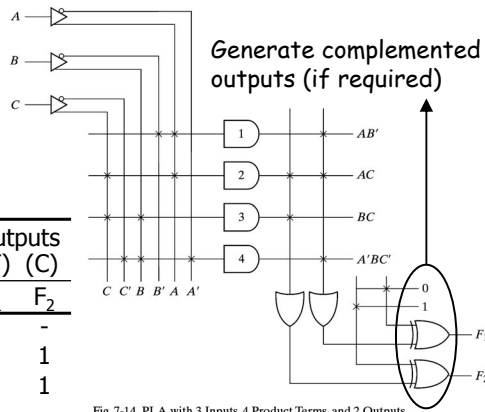

Product Term	Inputs			Outputs (T) (C)	
	A	B	C	F ₁	F ₂
AB'	1	0	-	1	-
AC	1	-	1	1	1
BC	-	1	1	-	1
A'BC'	0	1	0	1	-

Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

7-29

Implementation with PLA

- Example 7-2: implement the two functions with PLA
 - $F_1(A, B, C) = \Sigma(0, 1, 2, 4)$
 - $F_2(A, B, C) = \Sigma(0, 5, 6, 7)$
- Goal: minimize the number of **distinct** product terms between two functions

Product term	Inputs			Outputs	
	A	B	C	(C) F ₁	(T) F ₂
	AB	1	1	-	1
AC	1	-	1	1	1
BC	-	1	1	1	-
A'B'C'	0	0	0	-	1

A	BC		B	
	00	01	11	10
0	1	1	0	1
1	1	0	0	0

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

A	BC		B	
	00	01	11	10
0	1	0	0	0
1	0	1	1	1


$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C)'$$

7-30

Programmable Array Logic

 - PAL has a fixed OR array and a programmable AND array
 - Easier to program but not as flexible as PLA
- Each input has a buffer-inverter gate
- One of the outputs is fed back as two inputs of the AND gates
- Unlike PLA, a product term cannot be shared among gates
 - Each function can be simplified by itself without common terms




7-31

Implementation with PAL

$$w = \Sigma(2,12,13) \quad x = \Sigma(7,8,9,10,11,12,13,14,15)$$

$$y = \Sigma(0,2,3,4,5,6,7,8,10,11,15) \quad z = \Sigma(1,2,8,12,13)$$

Product Term	AND Inputs					Outputs
	A	B	C	D	W	
1	1	1	0	-	-	w = ABC'
2	0	0	1	0	-	+ A'B'CD'
3	-	-	-	-	-	
4	1	-	-	-	-	x = A
5	-	1	1	1	-	+ BCD
6	-	-	-	-	-	
7	0	1	-	-	-	y = A'B
8	-	-	1	1	-	+ CD
9	-	0	-	0	-	+ B'D'
10	-	-	-	-	1	z = w
11	1	-	0	0	-	+ AC'D'
12	0	0	0	1	-	+ A'B'C'D

 

7-32


Outline

- Introduction
- Random-Access Memory
- Memory Decoding
- Error Detection and Correction
- Read-Only Memory
- Combinational Programmable Devices
- **Sequential Programmable Devices**


7-33

Sequential PLD

 - The most simple sequential PLD = PLA (PAL) + Flip-Flops



 
- The mostly used configuration for SPLD is constructed with 8 to 10 macrocells as shown right



7-34

Complex PLD

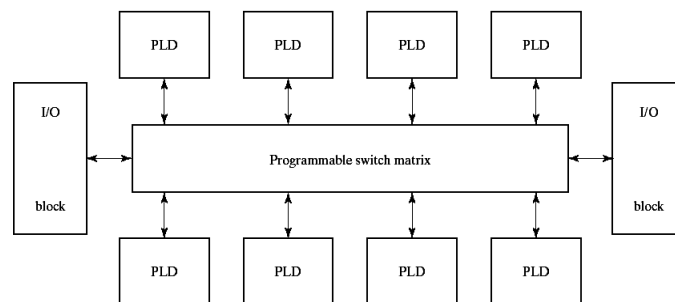- Complex digital systems often require the connection of several devices to produce the complex specification
 - More economical to use a complex PLD (CPLD)
- CPLD is a collection of individual PLDs on a single IC with programmable interconnection structure



7-35

Field Programmable Gate Array

- Gate array: a VLSI circuit with some pre-fabricated gates repeated thousands of times
 - Designers have to provide the desired interconnection patterns to the manufacturer (factory)
- A field programmable gate array (FPGA) is a VLSI circuit that can be programmed in the user's location
 - Easier to use and modify
 - Getting popular for fast and reusable prototyping
- There are various implementations for FPGA
 - More introductions are adopted from "Logic and Computer Design Fundamentals", 2nd Edition Updated, by M. Morris Mano and Charles R. Kime, Prentice-Hall, 2001

7-36

FPGA Structure (Altera)


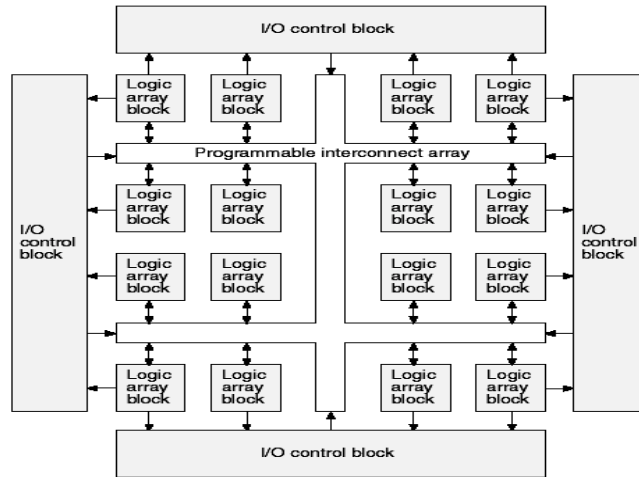


Fig. 6-28 Altera® MAX 7000™ Structure (Reprinted with Permission of Altera Corporation, © Altera Corp., 1991)

7-37


FPGA Structure (Xilinx)

 

7-38

Store the Programming Info.

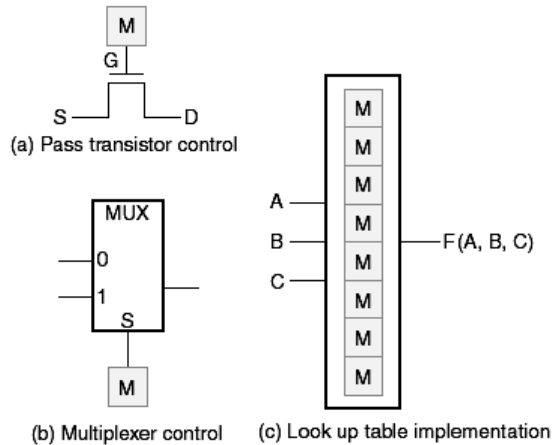
- SRAM technology is used
 - M = 1-bit SRAM
 - Loaded from the PROM after power on
- Store control values
 - Control pass transistor
 - Control multiplexer
- Store logic functions
 - Store the value of each minterm in the truth table



7-39

Xilinx FPGA Routing

 
- Fast direct interconnect
 - Adjacent CLBs
- General purpose interconnect
 - CLB – CLB or CLB – IOB
 - Through switch matrix
- Long lines
 - Across whole chip
 - High fan-out, low skew
 - Suitable for global signals (CLK) and busses
 - 2 tri-states per CLB for busses



7-40

Xilinx Switch Matrix

 - Six pass transistors to control each switch node
- The two lines at point 1 are joined together
- At point 2, two distinct signal paths pass through one switch node



(a) Switch Matrix Transistors


(b) Examples of Connections

Fig. 6-31 Example of Xilinx® Switch Matrix (Adapted with Permission of Xilinx®, Inc.)

7-41


Configurable Logic Block (CLB)

 - Combinational logic via lookup table
 - Any function(s) of available inputs
- Output registered and/or combinational



7-42

Simplified CLB Structure

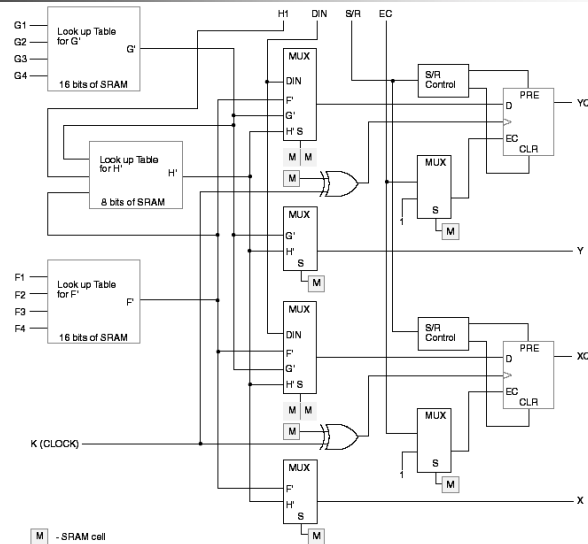

7-43

Internal Functions of a CLB

- Two 4-input tables implement two distinct functions (F' and G')
- F' and G' with another control ($H1$) feed into a third lookup table (H')
- Two arbitrary functions of up to four variables and selected functions of up to nine variables can be implemented
- Properly setting the two MUXes can assign any pair of F' , G' , and H' to the two combinational outputs (X and Y)

7-44


Internal Functions of a CLB

- Two D flip-flops directly drive outputs XQ and YQ
- Each of the D inputs can be selected from F', G', H' and input DIN
- Two XORs select each flip-flop individually to be positive or negative edge triggered
- Two SR controls select the signal S/R to be an asynchronous Set or Reset for the flip-flops
- Two multiplexers allow the input EC to optionally act as a clock ENABLE signal for each flip-flop

7-45

I/O Block (IOB)

 
- Periphery of identical I/O blocks
 - Input, output, or bidirectional
 - Registered, latched, or combinational
 - Three-state output
 - Programmable output slew rate



7-46

Input/Output Mode of an IOB

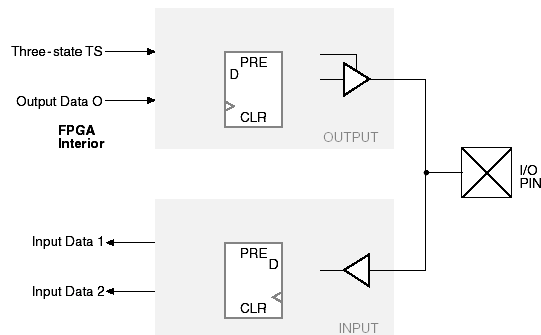- Input
 - 3-state control places the output buffer into high impedance
 - Direct in and/or registered in
- Output
 - 3-state driver should be enabled by TS signal
 - Direct output or registered output




7-47

Design with FPGA

- Using HDL, schematic editor, SM chart or FSM diagram to capture the design
- Simulate and debug the design
- Work out detail logic and feed the logic into CLBs and IOBs
 - Completed by a CAD tool
- Generate bit pattern for programming the FPGA and download into the internal configurable memory cells
- Test the operations

7-48


FPGA Design Flow

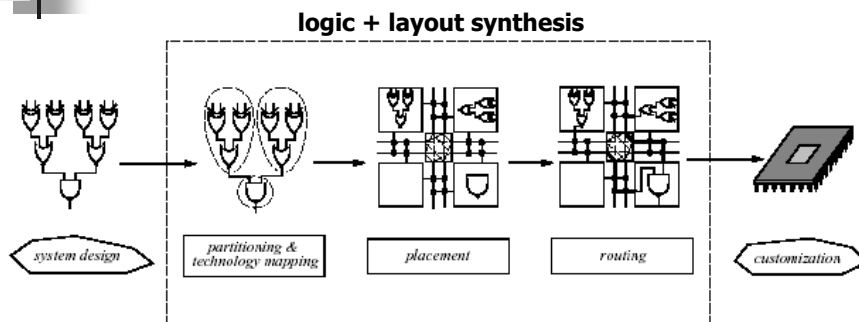

- Advantages: Fast and reusable prototyping
 - Can be reprogrammed and reused
 - Implementation time is very short
- Disadvantages: Expensive and high volume

7-49

Download to a FPGA Demo Board

 

Source: CIC training manual

7-50